

- ① Derive amplification formulas for Inverting Amplifier, Non inverting amplifier, Difference amplifier and Instrumentation Amplifier. (10)

- ② Consider following truth-table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

(10)

Find boolean expression for S as well as C using product-of-sums method and sum-of-products method.

- ③ Design a boolean circuit for a security protection system. Alarm should sound if someone breaks into house through a door/window or if something is moving around in the house while the occupants are away. Write Quasi-logic statements, boolean expression, truth table and boolean circuit (using only AND gates/NOT gates).

(10)