

1. Derive expression for rms value and average value of alternating current.
2. Write short notes on:-
 - (i) Zener diode (ii) Impedance matching
 - (iii) Transistor as a switch (iv) Field-Effect Transistor

3.

